

# Passive Neuronal Membrane

Computational Neuroscience by University of Washington

The following Python code models a passive neuronal membrane as an RC-circuit. (Remember that in the membrane model, the resistor and capacitor are in parallel.)

Python (all versions):

`membrane.py`

This code demonstrates how a membrane responds to a constant current input that is turned on for a fixed time interval and then turned off.

## Part A

What if the current were not turned off? What would the steady state voltage of the membrane be? Use the values given in the script to compute your answer ( $C = 0.1$  nF,  $R = 100$  M $\Omega$ ,  $I = 10$  nA). You should give your answer in mV. Do not include units in your answer.

## Part B

Change the values for the membrane's resistance and capacitance ( $R$  and  $C$ ), and find out how this influences the response of the membrane. Does it reach a stable value more quickly or more slowly after multiplying  $R$  by 5?

## Part C

Does it reach a stable value more quickly or more slowly after dividing  $C$  by 10?

## Part D

Does it reach a stable value more quickly or more slowly after multiplying  $R$  by 10 AND dividing  $C$  by 10?